

# Single Phase Unipolar PWM Inverter

## 1 Objective:

To simulate the Single Phase Full Bridge Inverter with Unipolar PWM technique in MATLAB/SIMULINK.

### 1.1 Design specifications:

- Input Voltage ( $V_{in}$ ): 350 V
- Peak value of triangular voltage : 10 V
- Frequency of triangular signal : 1KHz
- Load Resistor ( $R$ ): 50  $\Omega$
- Load Inductor ( $L$ ): 50 mH;
- Control signal ( $V_{cont}$ ):  $6\sin(2*50\pi t)$

## 2 Unipolar PWM Technique:

- One leg is controlled with  $V_{cont}$  and another with  $-V_{cont}$ .
- When  $V_{cont} \cdot V_{tri} \rightarrow$  T1 is ON, and When  $V_{cont} < V_{tri} \rightarrow$  T4 is ON.
- When  $-V_{cont} \cdot -V_{tri} \rightarrow$  T2 is ON, and When  $-V_{cont} < -V_{tri} \rightarrow$  T3 is ON.
- Output voltage ( $V_0$ ) =  $m_a(V_{in})\sin(nw_0t)$
- Total harmonic distortion ( $THD$ ) :  $\sqrt{\frac{V_{rms}^2 - V_1^2}{V_1^2}} = 6.27\%$

### 3 Simulation Diagram :

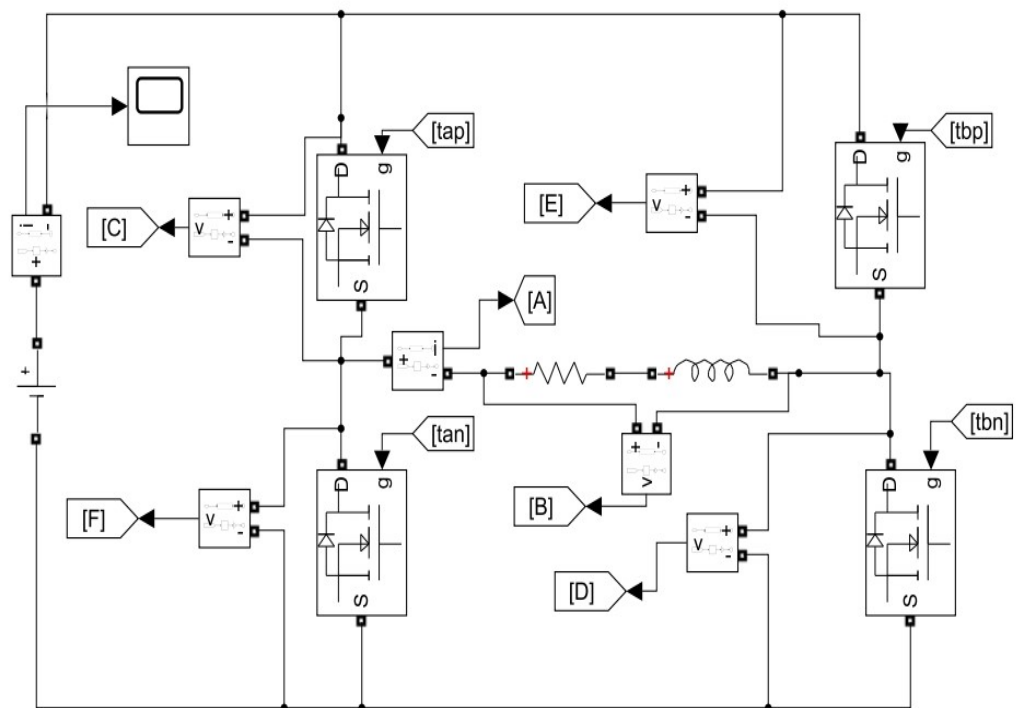
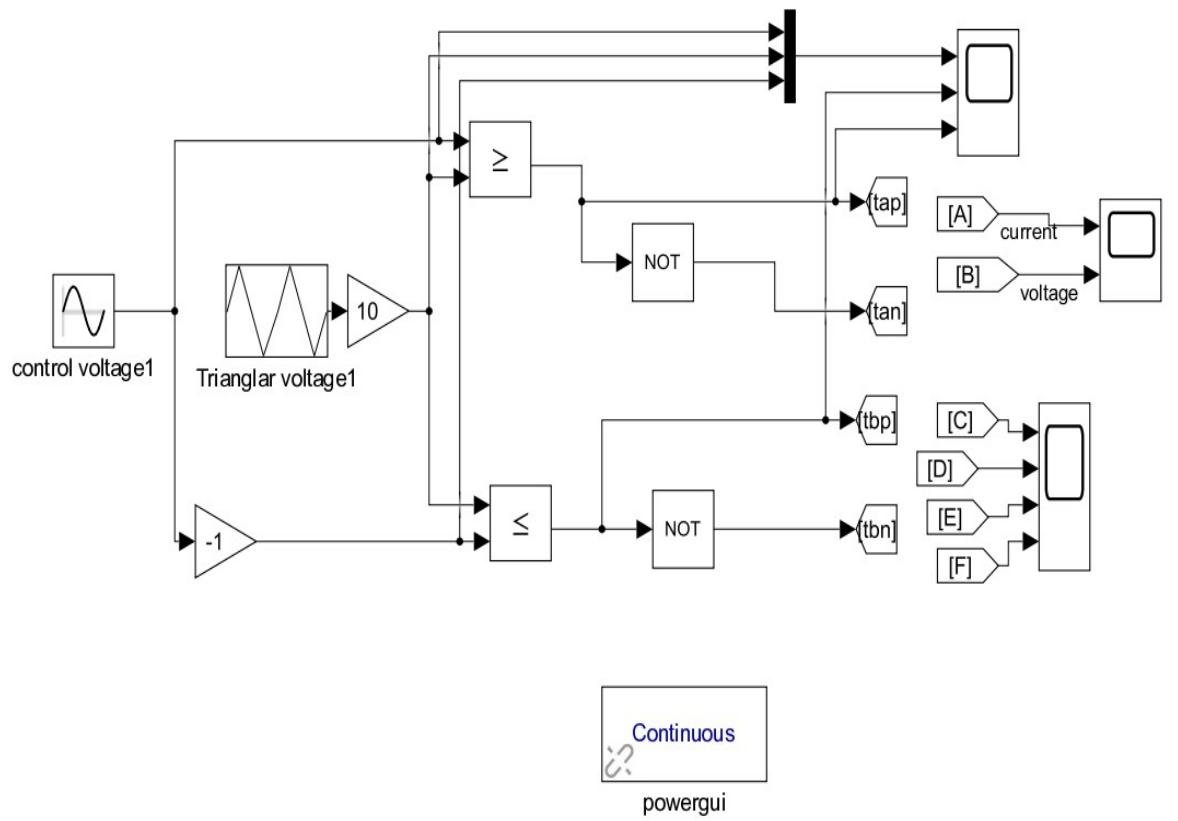


Fig. 1: Simulink Model

## 4 Waveforms

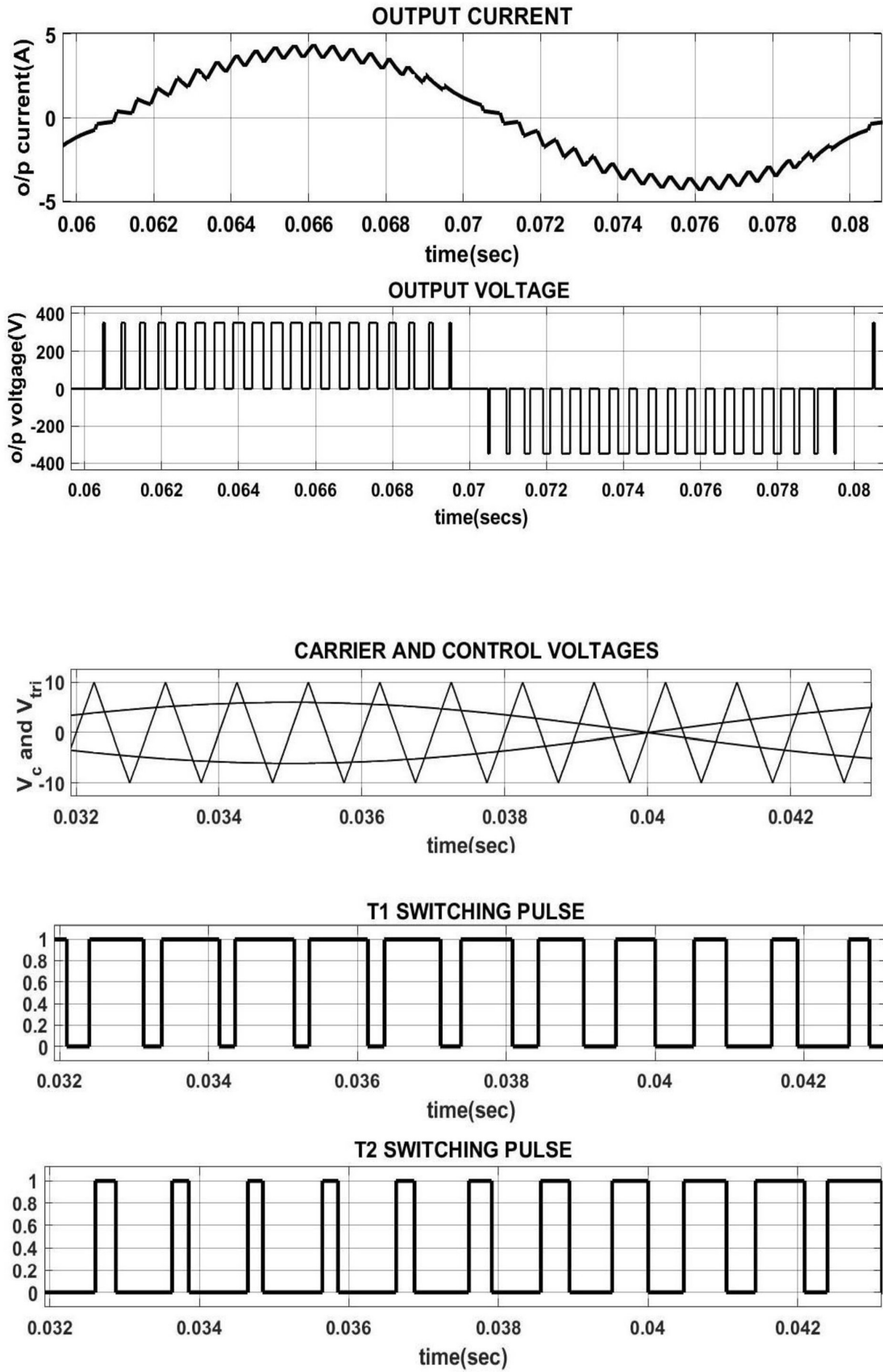


Fig. 2: Output voltage and Output current waveforms

## 4.1 Harmonics spectrum

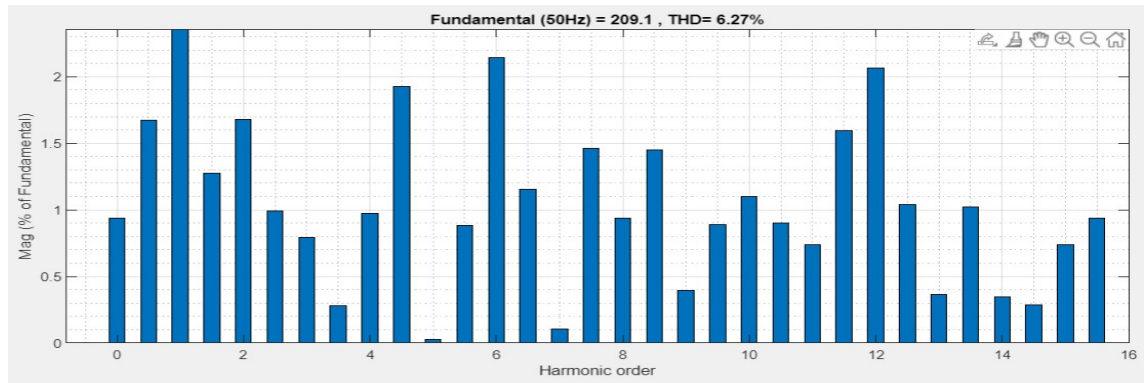


Fig. 3: Harmonics spectrum of Load voltage